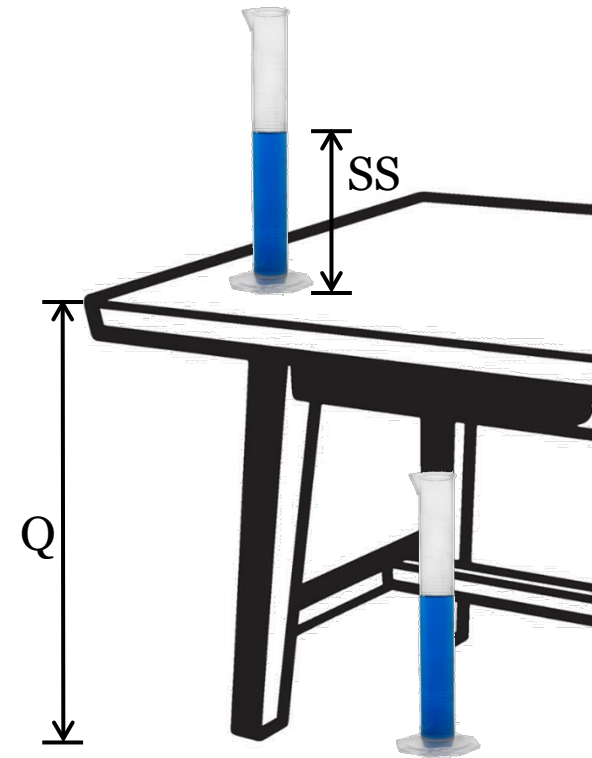


1.3 – DC Operating Point and Signal Variation


Analyzing Real Circuits

- Real circuits have:
 - A DC Operating Point (Q)
 - A Small-Signal (SS) response (linear only)
 - Often neglect nonlinear AC effects
- Why?
 - To keep signals within the voltage rails
 - Example: A physics experiment (SS) on top of a table (Q) instead of the floor
 - Sometimes the circuit response to SS depends on Q
 - Example: Turning on a gasoline engine (Q) then revving it (SS)




Decomposing Circuit Response

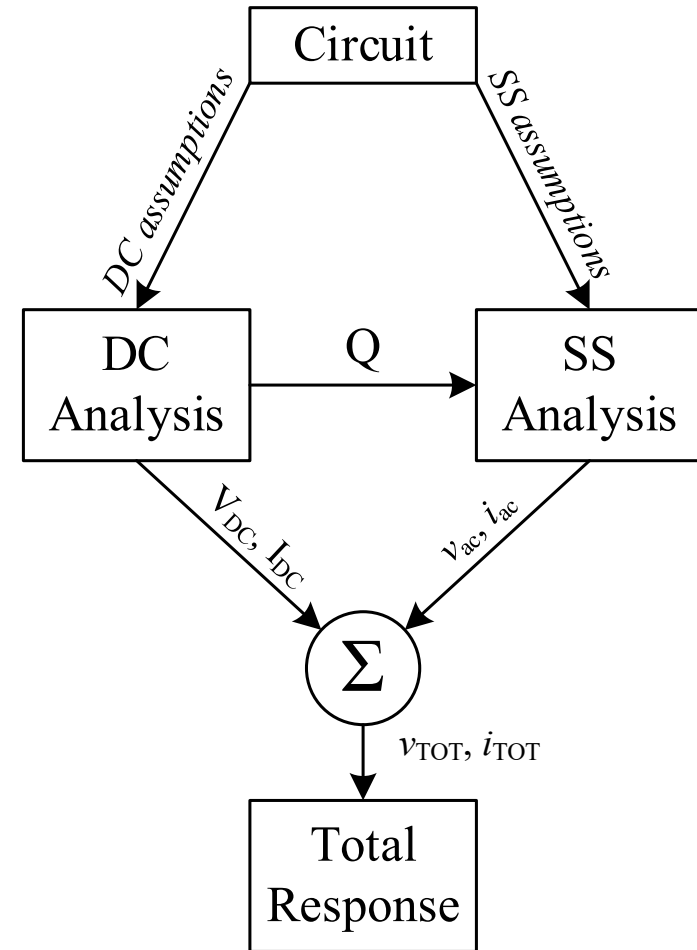- Draw a DC version of the circuit
 - Determine Q
- Draw a SS version of the circuit
 - Determine SS response
- Sum the responses to get the total response



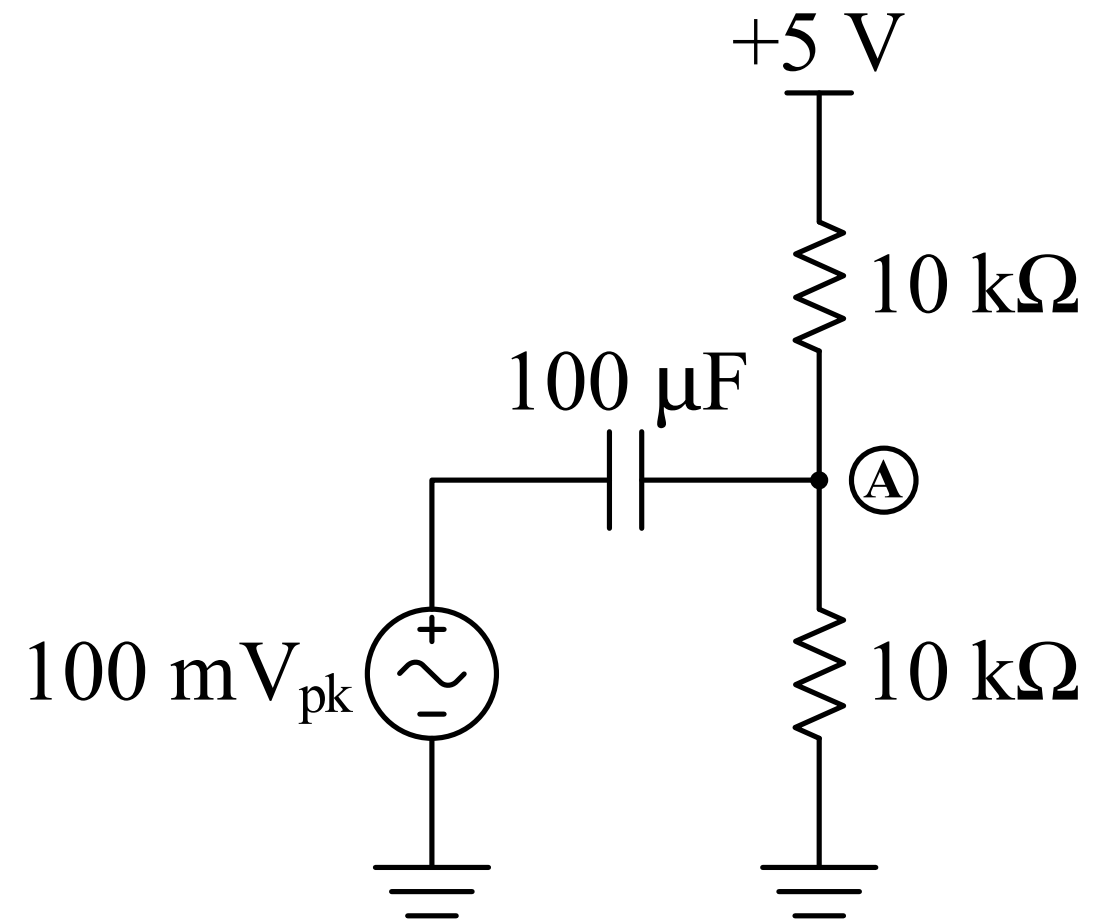Example


- Determine v_A , the total response of this circuit



Redraw Circuit for DC and SS Analysis



DC:

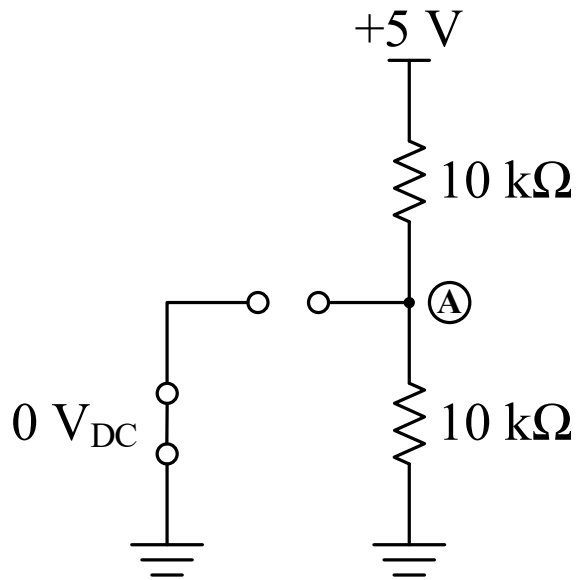- $C \rightarrow \text{open}$
- $L \rightarrow \text{short}$
- $v_{ac} \rightarrow 0 \text{ V}_{DC} \rightarrow \text{short}$
- $i_{ac} \rightarrow 0 \text{ I}_{DC} \rightarrow \text{open}$






SS (AC):

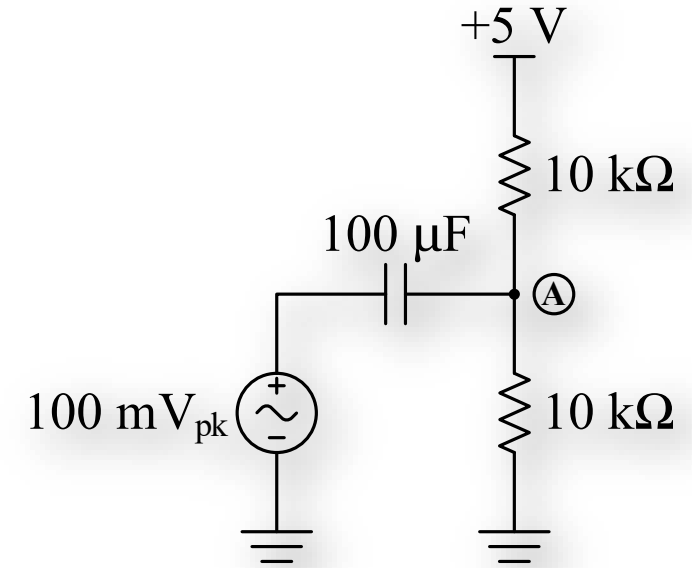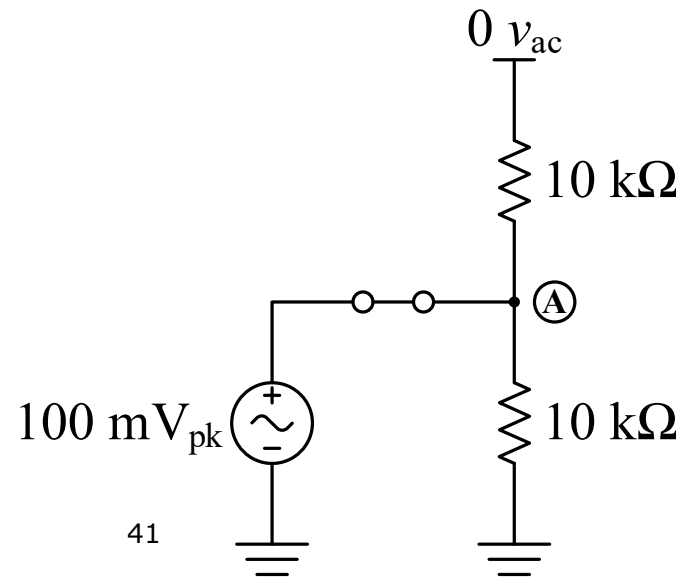
- $C \rightarrow \text{short}$
- $L \rightarrow \text{open}$
- $V_{DC} \rightarrow 0 \text{ } v_{ac} \rightarrow \text{short}$
- $I_{DC} \rightarrow 0 \text{ } i_{ac} \rightarrow \text{open}$



Sum to get Total Response

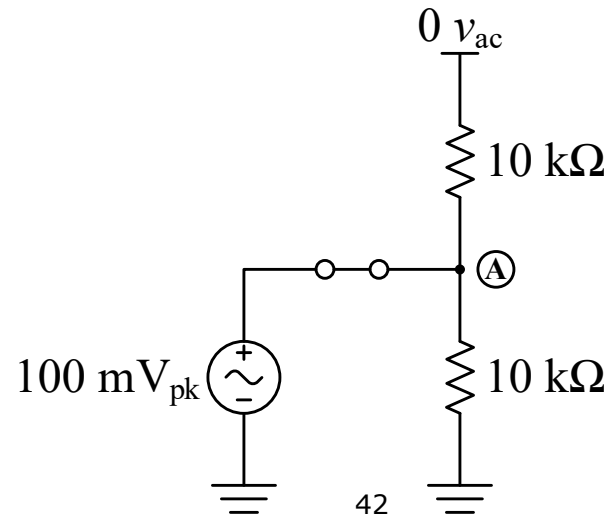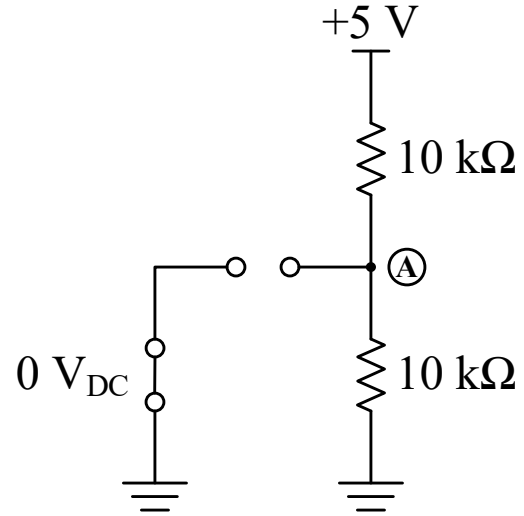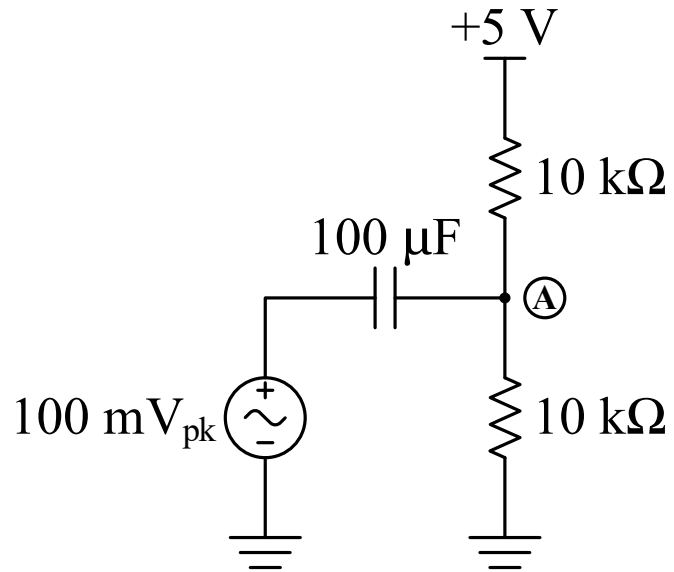

LTSpice Modeling Challenge

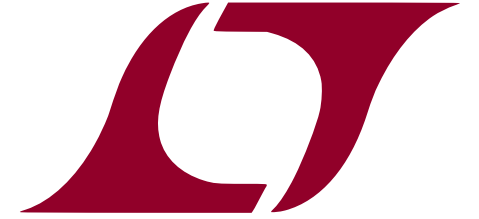

- Create the example circuit schematic
 - Perform a DC analysis (“DC op pnt”)
 - Perform a transient analysis (choose a frequency for your 100 mV source)
- How could you find only the AC response?
- What does the AC Analysis do, and how is that different?
- What happens if you change the value of C?

