



2.3 – Diodes



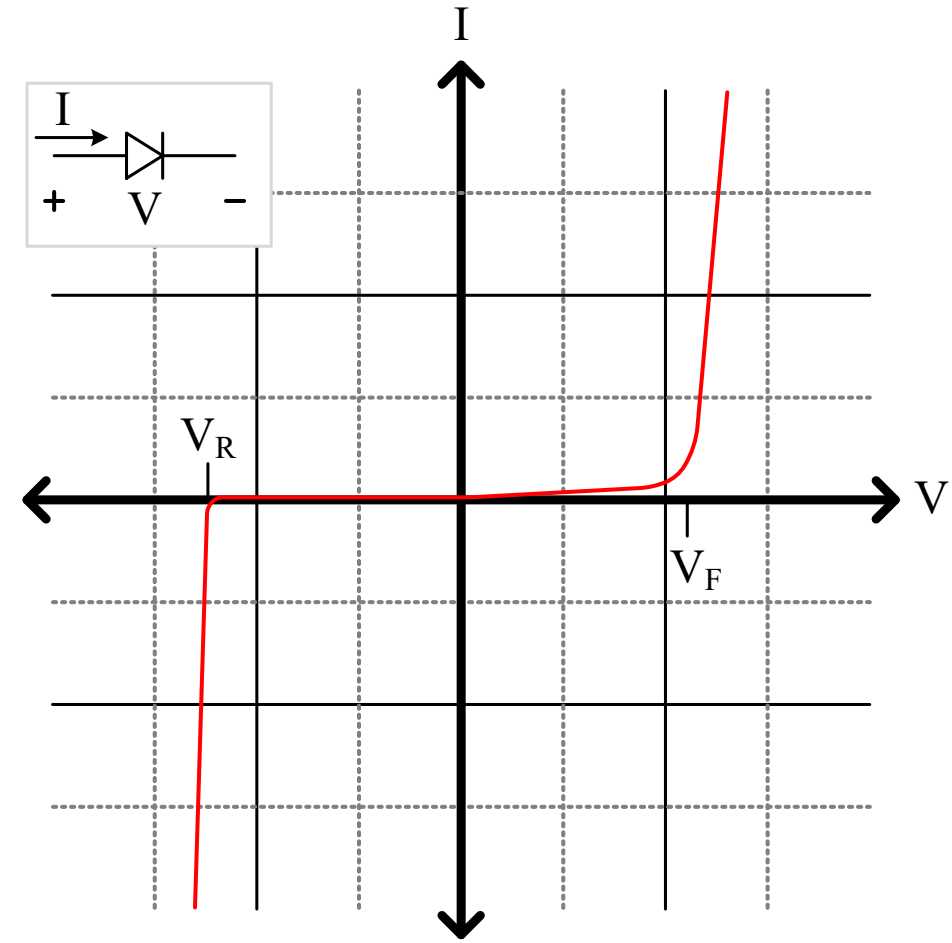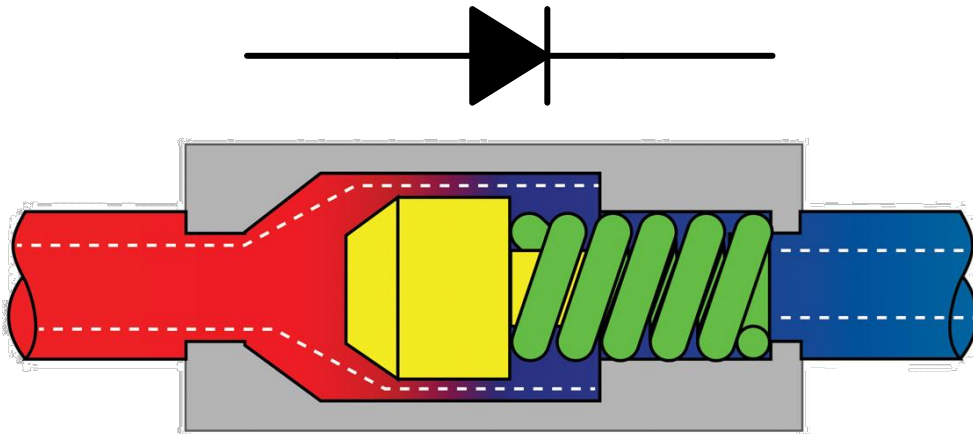2.3.1 – Diode Operation and Circuit Model

Diodes are Like One-way Valves

- No flow until you push hard enough
- Blocks reverse flow... until it breaks!
- Like a check valve







<https://youtu.be/7ukDKVHnac4?si=s24e4jpI8bClEqjW&t=45>



Diode Models


Rather than full exponential model,
use ON/OFF model:

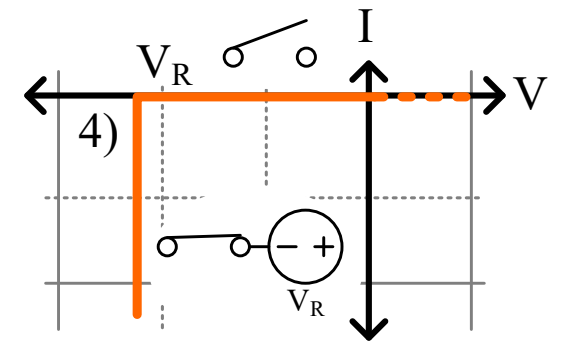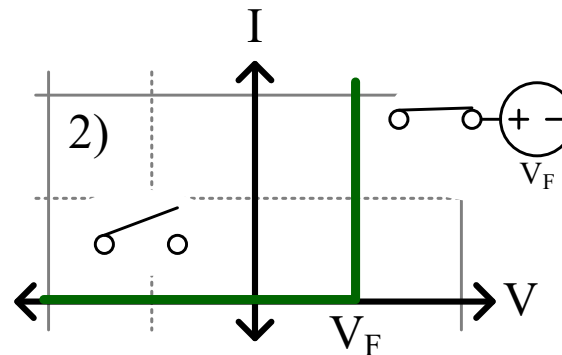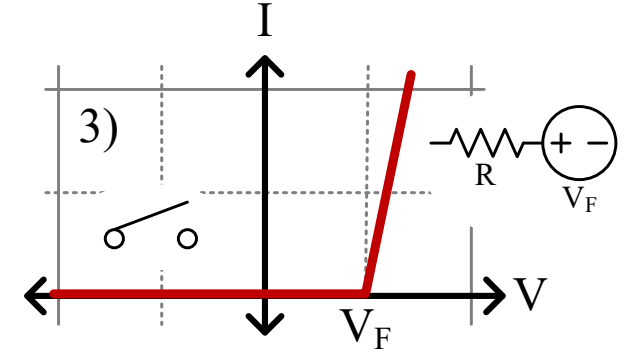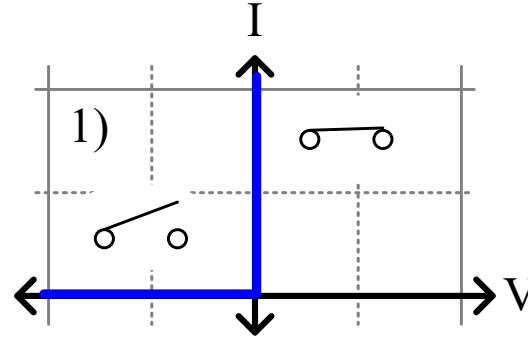- 1) Simple switch
- 2) Switch with an offset voltage
- 3) Switch with offset voltage and resistance
- 4) Include reverse breakdown




Diode Analogy

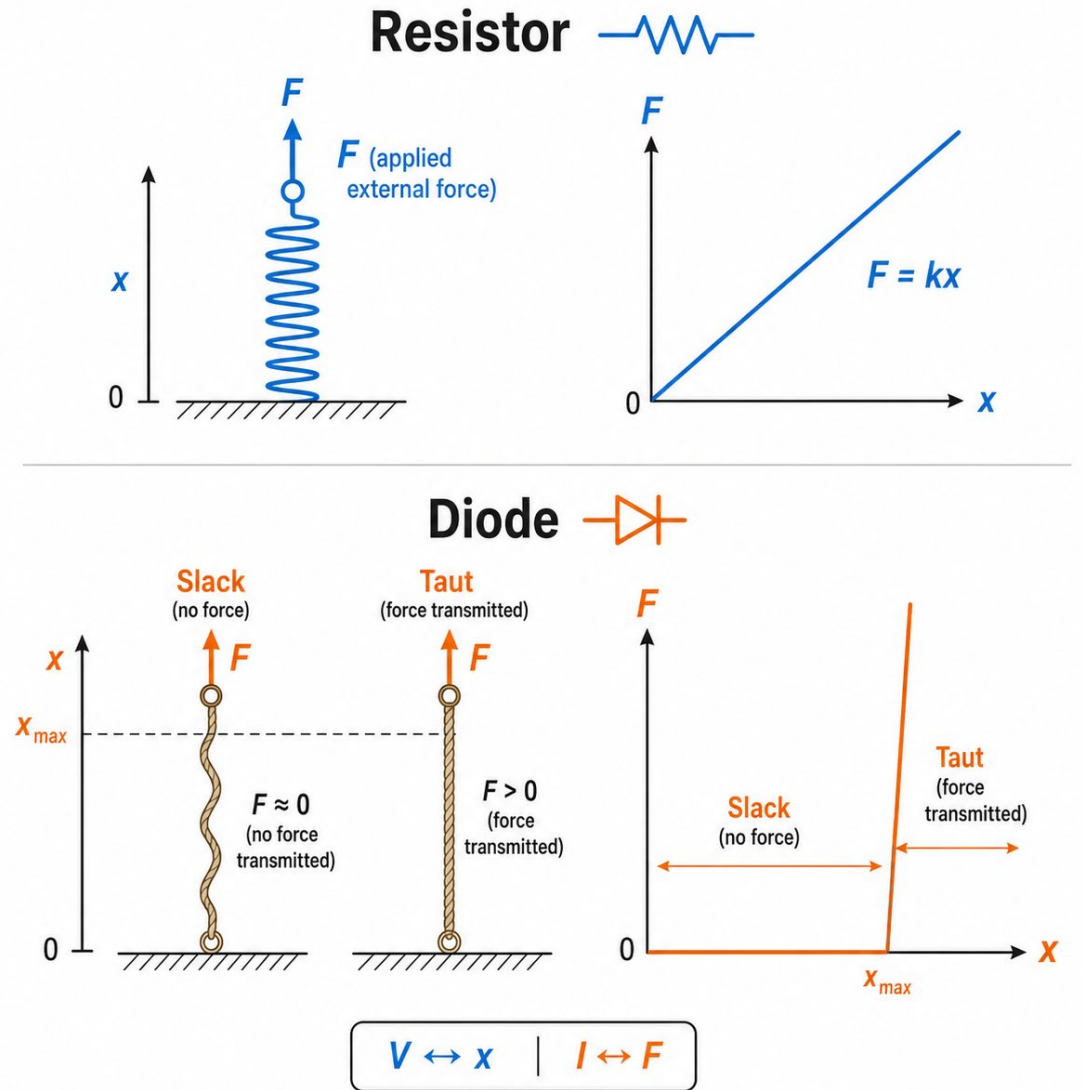
- Think about voltage V as a vertical position x
- Think about current I as an applied force F
- A **resistor** is like a **spring**:
 - Position and force are proportional
- A **diode** is like a **rope**:
 - No force until max position
 - Then, position mostly fixed for any force



Diode Circuit Behaviour – Example 1

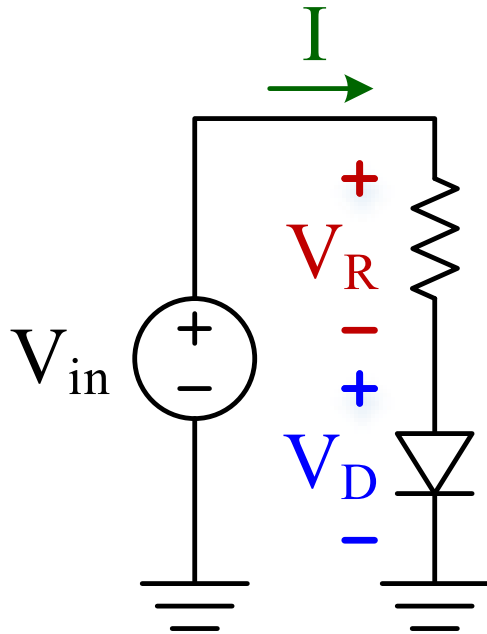

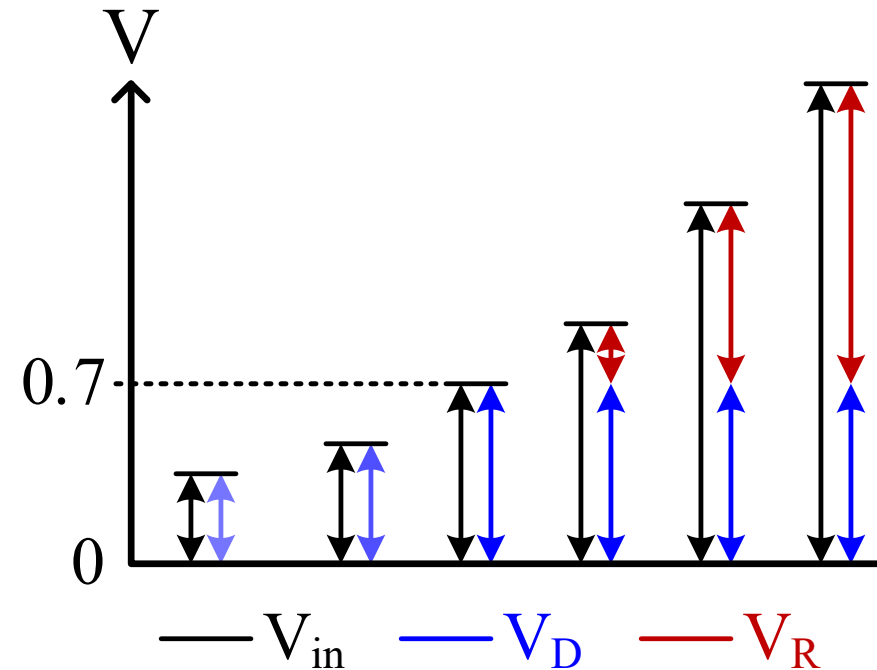
This diode turns ON at 0.7 V
Called V_F : Forward Voltage




<https://everycircuit.com/circuit/5715452701179904>



Diode Circuit Behaviour – Example 2

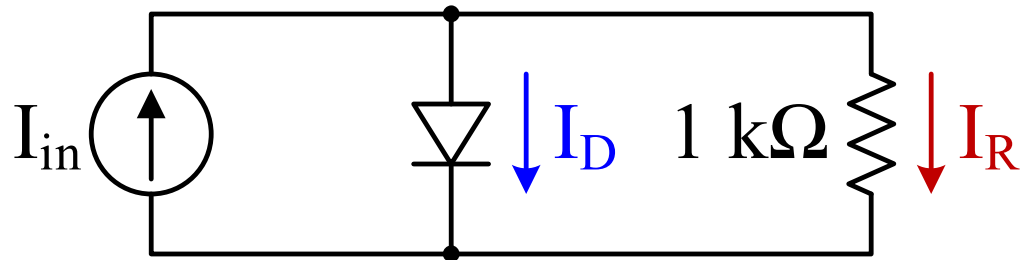

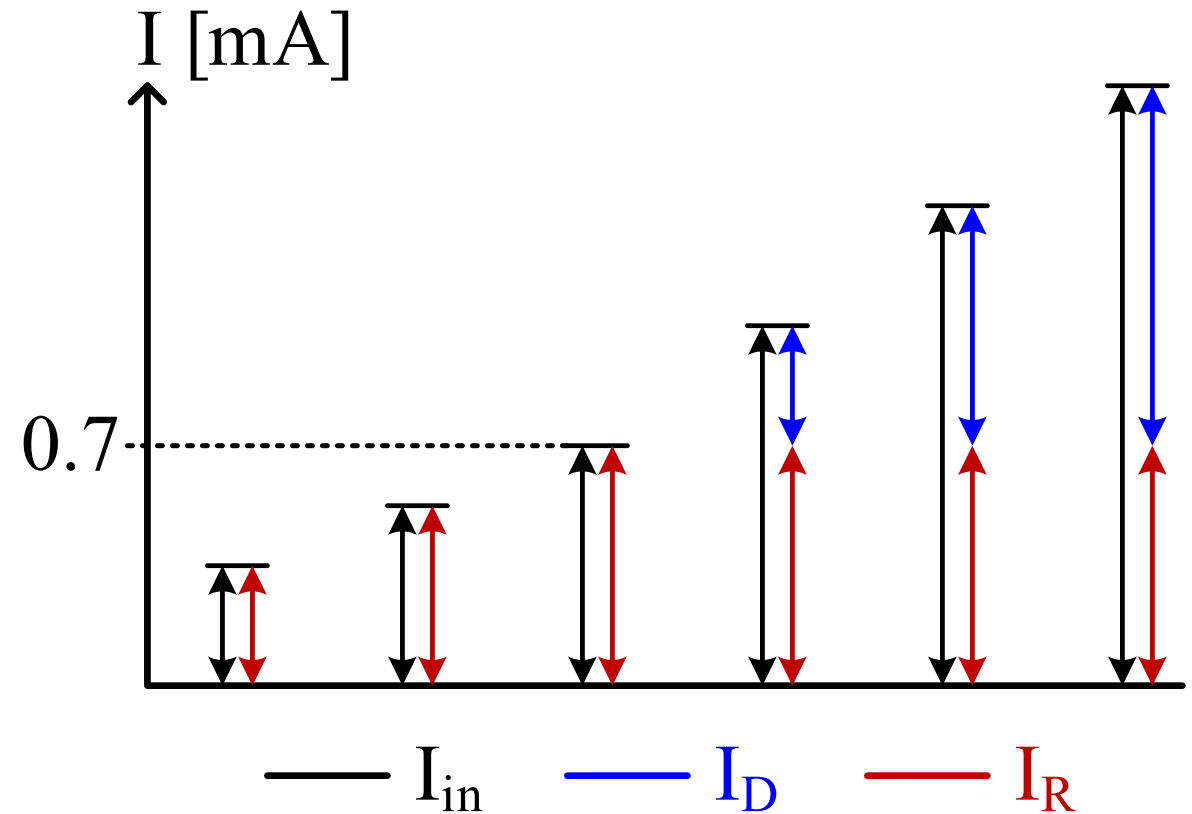This diode turns ON at 0.7 V
(when $I_{in} \times R = 0.7\text{ V}$)



<https://everycircuit.com/circuit/5219441801560064>





2.3.2 – Diode Types

Diode Types: PN Junction

- “Normal” diode. E.g., pervasive 1N4148 diode:



ELECTRICAL CHARACTERISTICS (Values are at $T_A = 25^\circ\text{C}$ unless otherwise noted) (Note 2)

Symbol	Parameter		Conditions	Min	Max	Unit
V_R	Breakdown Voltage		$I_R = 100\ \mu\text{A}$	100		V
			$I_R = 5.0\ \mu\text{A}$	75		V
V_F	Forward Voltage	914B / 4448	$I_F = 5.0\ \text{mA}$	0.62	0.72	V
		916B	$I_F = 5.0\ \text{mA}$	0.63	0.73	V
		914 / 916 / 4148	$I_F = 10\ \text{mA}$		1.0	V
		914A / 916A	$I_F = 20\ \text{mA}$		1.0	V
		916B	$I_F = 20\ \text{mA}$		1.0	V
		914B / 4448	$I_F = 100\ \text{mA}$		1.0	V
I_R	Reverse Leakage		$V_R = 20\ \text{V}$		0.025	μA
			$V_R = 20\ \text{V}, T_A = 150^\circ\text{C}$		50	μA
			$V_R = 75\ \text{V}$		5.0	μA
C_T	Total Capacitance	916/916A/916B/4448	$V_R = 0, f = 1.0\ \text{MHz}$		2.0	pF
		914/914A/914B/4148	$V_R = 0, f = 1.0\ \text{MHz}$		4.0	pF
t_{rr}	Reverse Recovery Time		$I_F = 10\ \text{mA}, V_R = 6.0\ \text{V} (600\ \text{mA})$ $I_{rr} = 1.0\ \text{mA}, R_L = 100\ \Omega$		4.0	ns






Diode Types: Light Emitting Diodes

- LED brightness proportional to forward current, I_F
 - 20 mA max typical setpoint
- V_F dependent on LED colour and is poorly controlled
 - Sometimes ± 0.5 V
- R sets current by dropping remaining voltage
 - $V_R = V_{DD} - V_F$, and $I_F = V_R/R$
 - Add enough voltage overhead to deal with V_F uncertainty
- Closed-loop feedback can provide a precise current independent of V_F (Transconductance Amplifier – OTA)

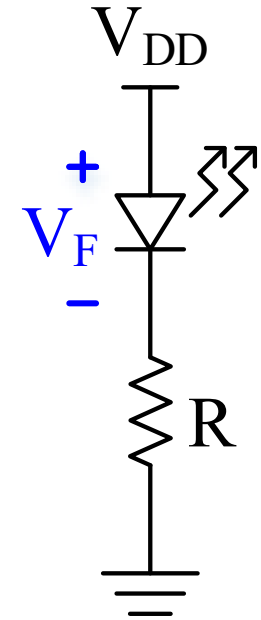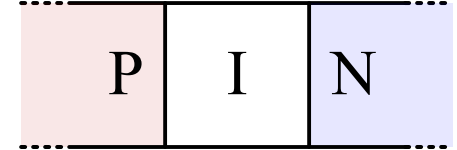



Diode Types: Photodiode

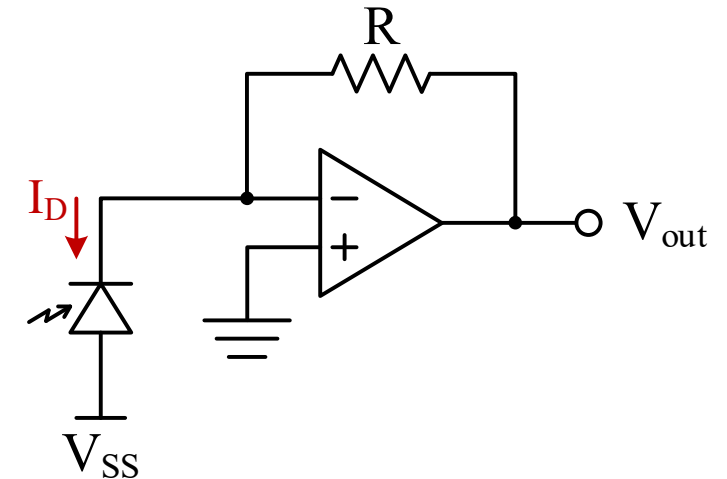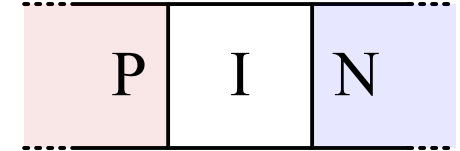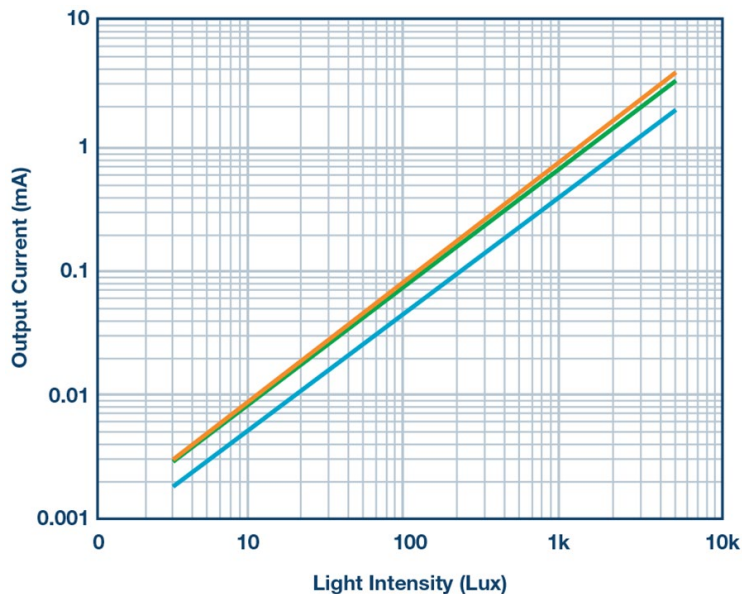- “Opposite” of an LED
- Allows reverse current flow when photons hit the depletion region
- Reverse current (I_D) proportional to illuminance:



Diode Types: Zener Diodes

- V_F is poorly controlled
- V_R can be well-controlled → Use as a voltage reference
- Zener diodes operate on the edge of reverse breakdown to provide a reasonably precise voltage reference
 - Given a specified I_Z , a Zener diode will drop V_Z across it
 - Choose a precision resistor, R , to drop the rest of the voltage
- Looks “backwards” – it is because we want to use V_R , not V_F
- Analyze just like a regular diode, using V_Z instead of V_F


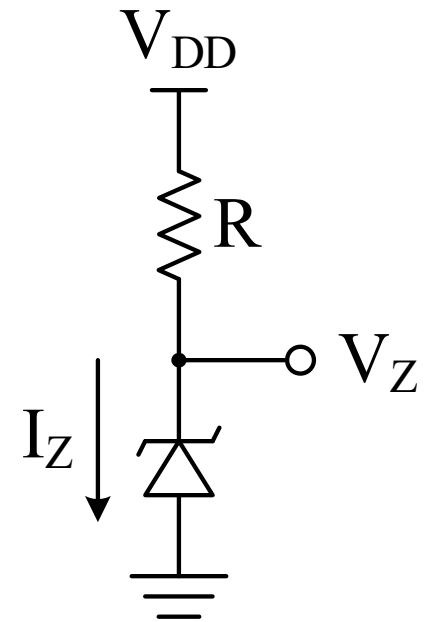
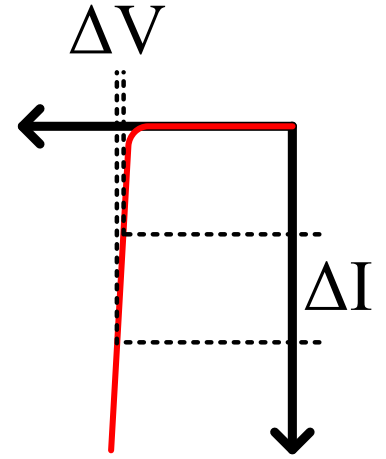




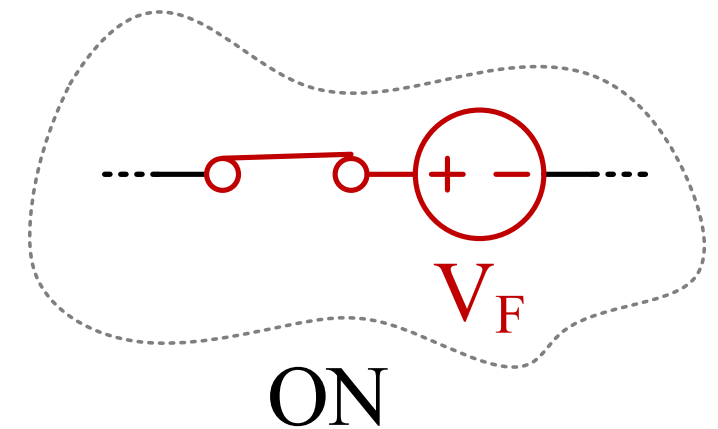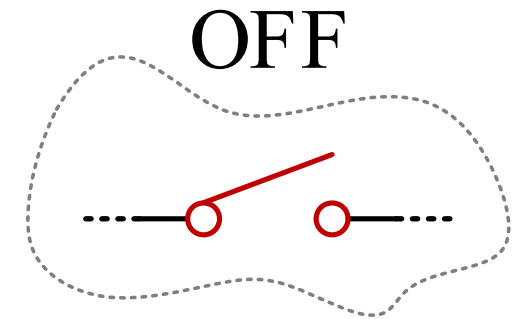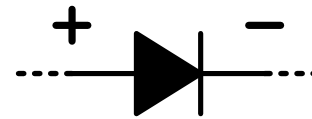2.3.3 – Diode Analysis Techniques


Diode Circuit Analysis – ON/OFF Model

- Use two models: OFF & ON
- Draw circuit with diode OFF
 - Solve for V_D and any other unknowns
- Draw circuit with diode ON
 - Solve for V_D and any other unknowns
- Use OFF model when $V_D < V_F$ and ON model when $V_D \geq V_F$




Diode Circuit Analysis Example

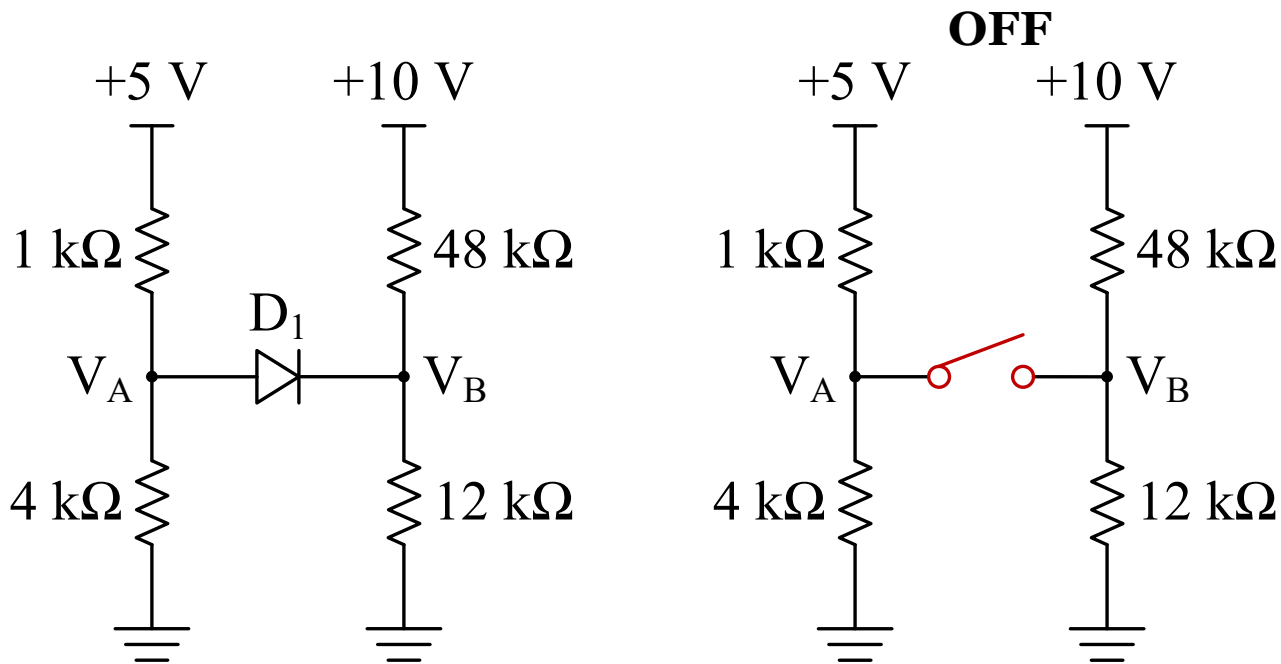- Determine V_A and V_B . Use a basic diode model that does not conduct any current until 0.7 V is applied, at which point it conducts any amount of current.






Diode Circuit Analysis Example

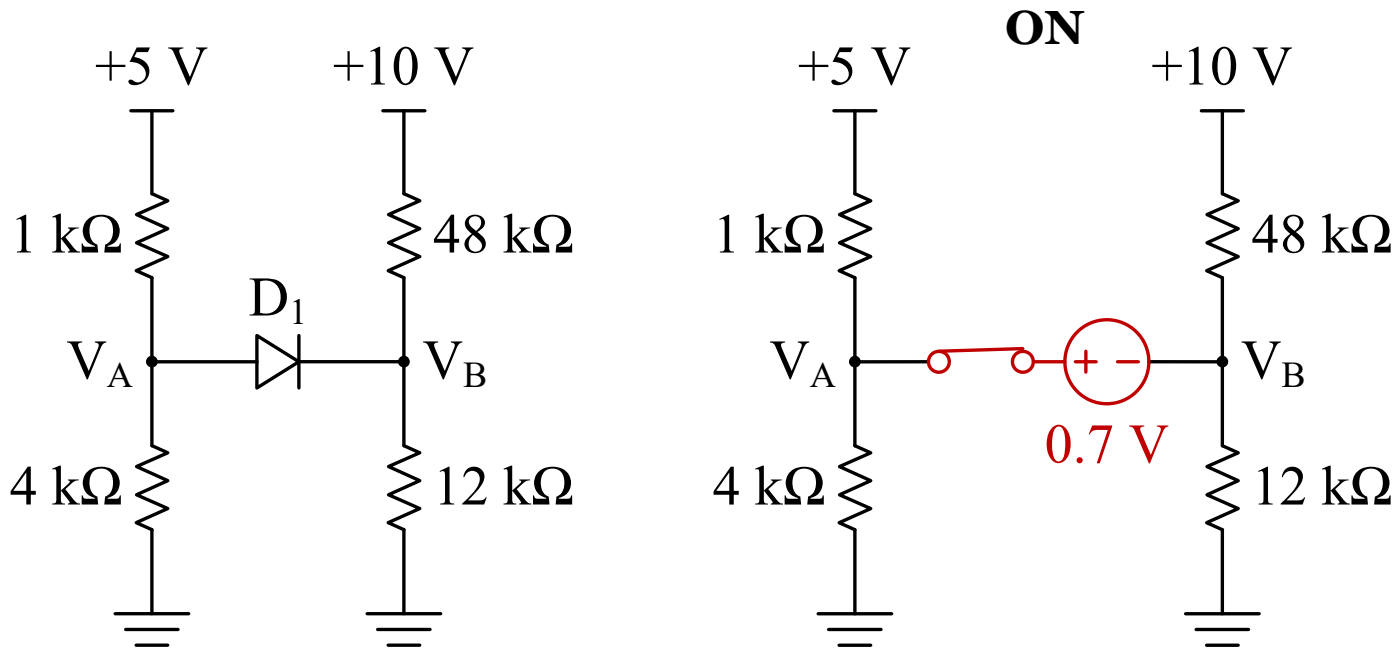- Determine V_A and V_B . Use a basic diode model that does not conduct any current until 0.7 V is applied, at which point it conducts any amount of current.




Diode Circuit Analysis Example: DC Sweep

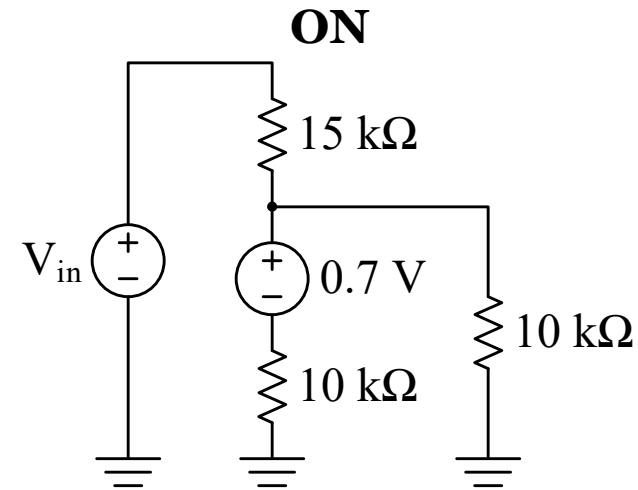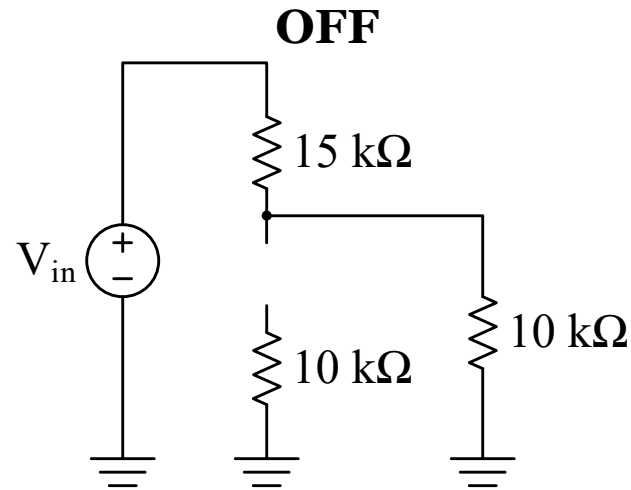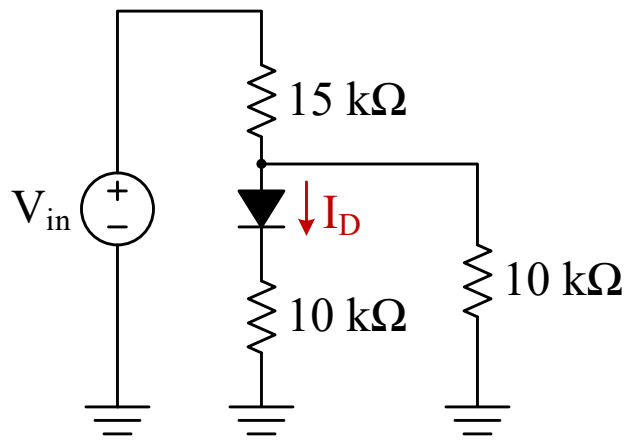- Plot V_{D+} , V_{D-} , V_D , and I_D for V_{in} from 0 to 5 V. Use the same basic diode model.




Diode Circuit Analysis Example: DC Sweep

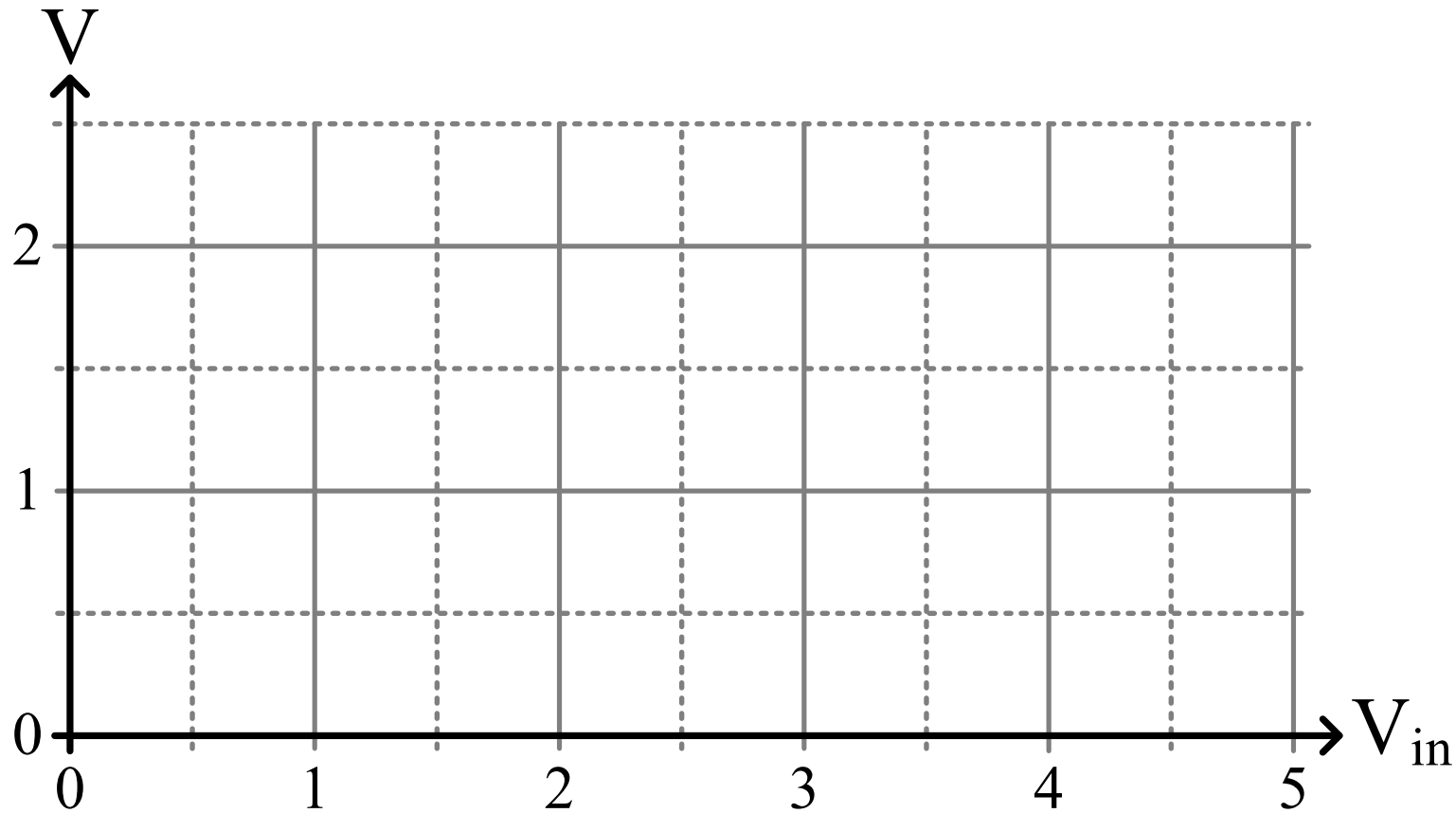

2.3.4 – Diode Circuits

Rectifiers

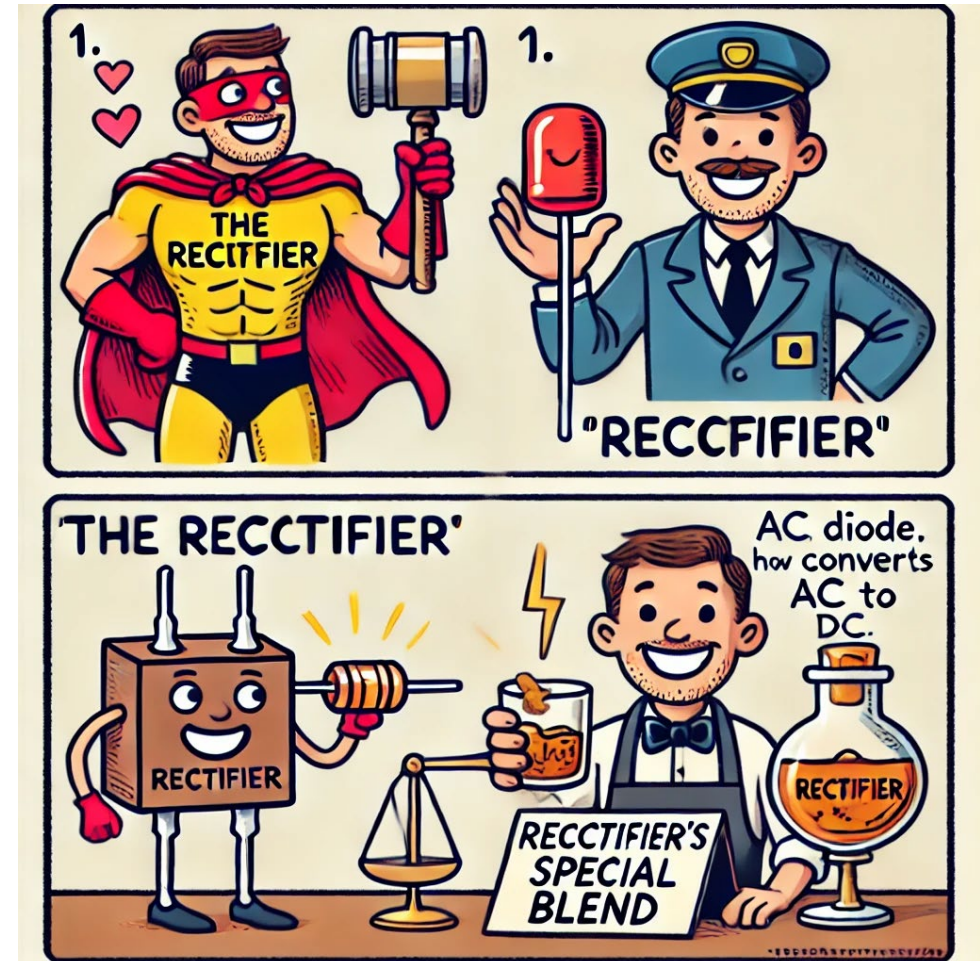1. One that rectifies: a rectifier of many wrongs.
2. Electronics: A device, such as a diode, that converts alternating current to direct current.
3. A worker who blends or dilutes whiskey or other alcoholic beverages.





ChatGPT's best efforts in 2024




Diode Circuits: Half-Wave Rectifier

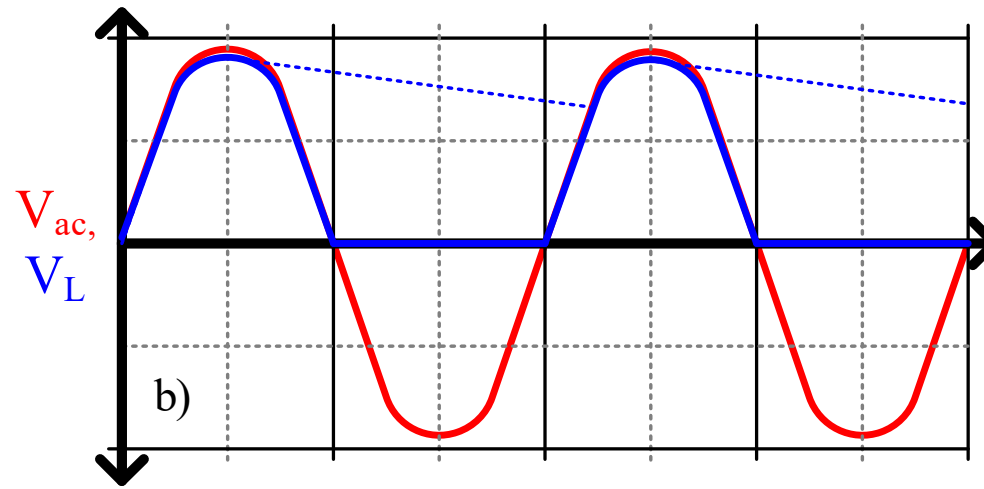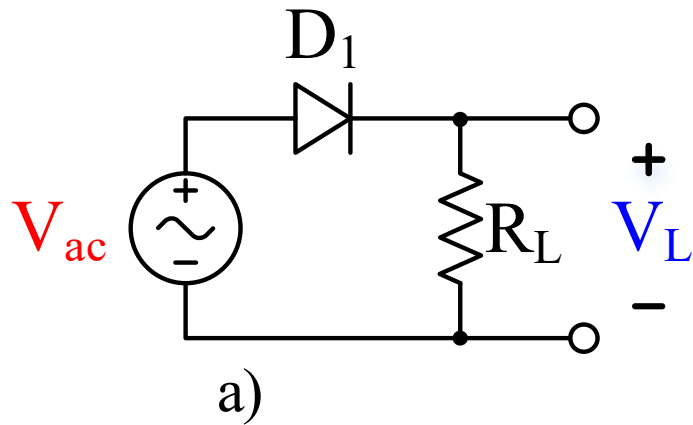- You can turn AC into DC with diodes
- Half-wave rectifier only lets the positive part of the AC cycle through
- Can add a large capacitance to smooth it out (Bulk Decoupling Capacitor)
 - Reduces the ripple





Diode Circuits: Full-Wave Rectifier


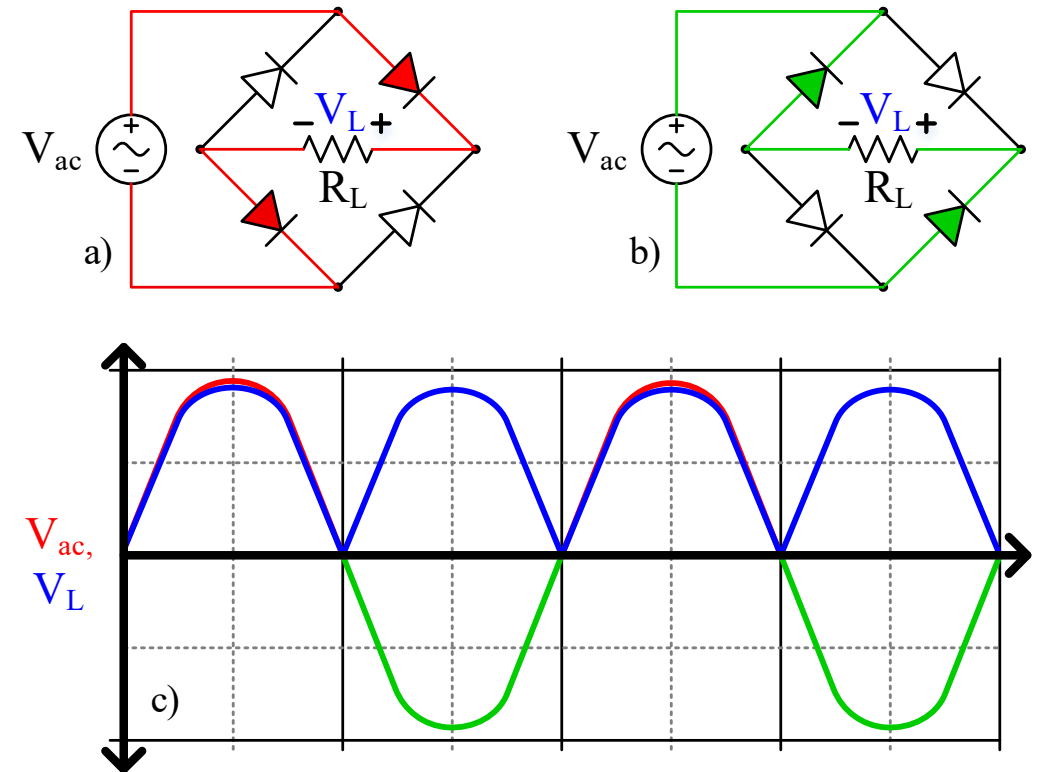
- A full-wave rectifier does a better job
- Also called **bridge rectifier**
- Two diodes ON for positive cycle
Two diodes ON for negative cycle
- Routes current through the load in the same direction both times
- Again, can add a big capacitor to reduce the ripple



Peak Detector

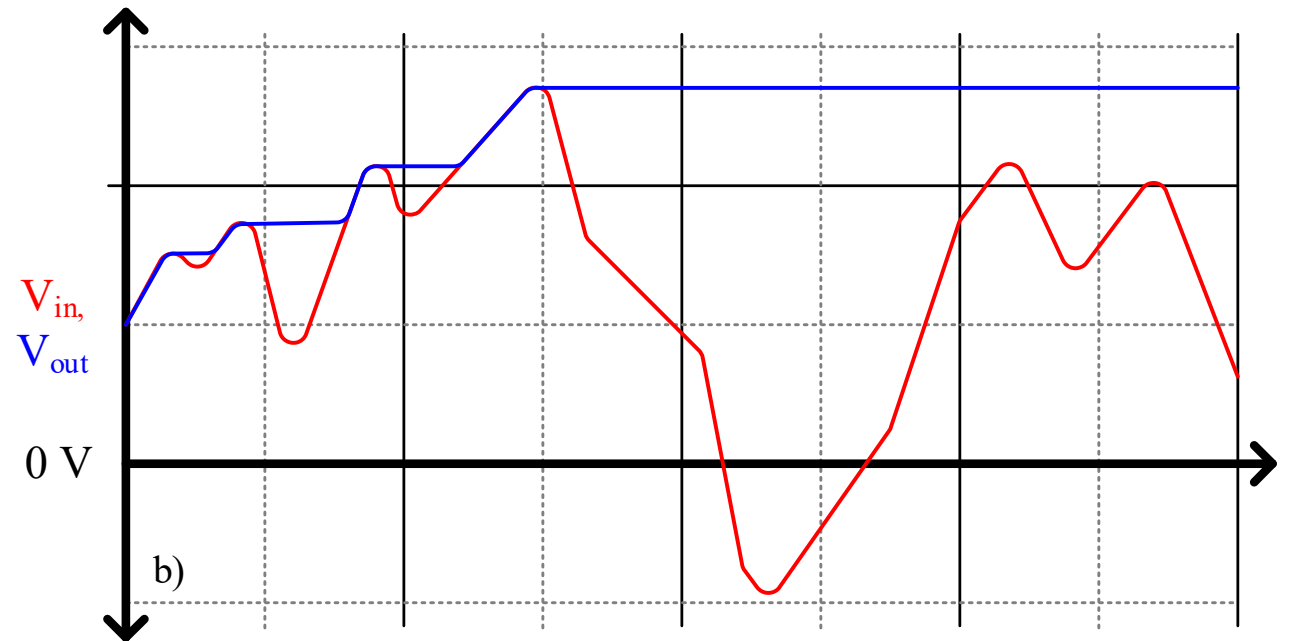
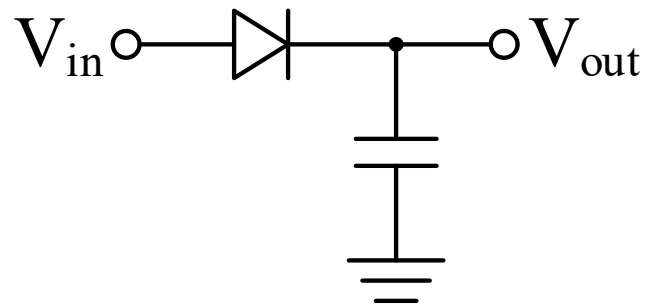


Envelope Detector

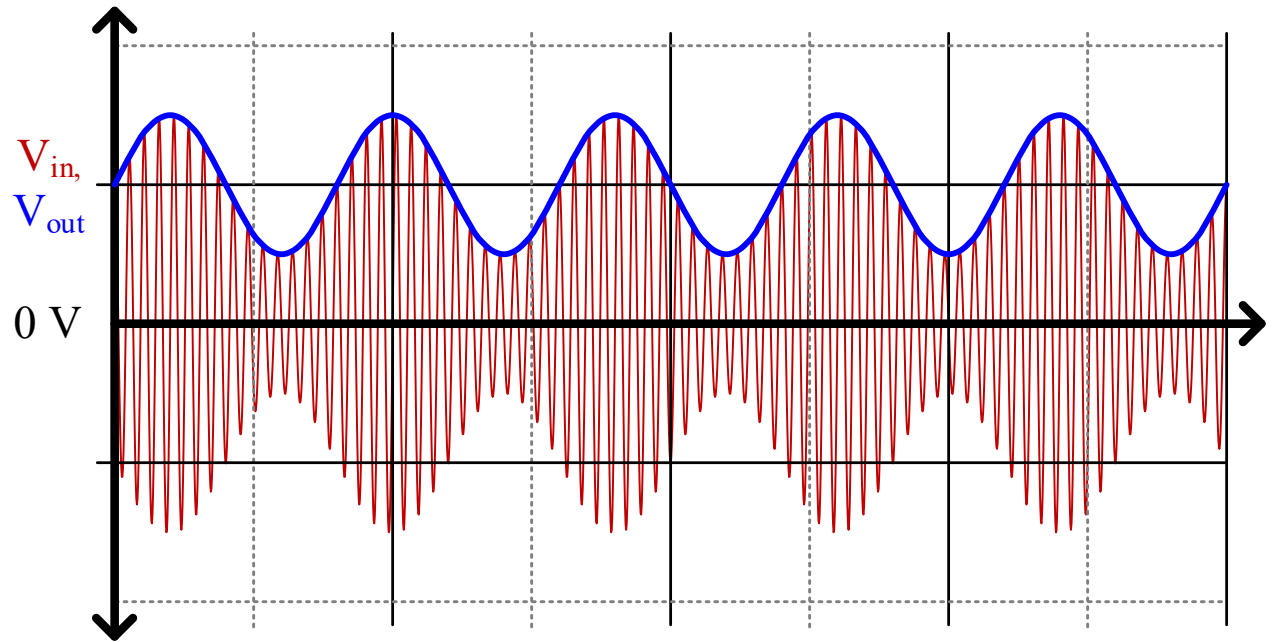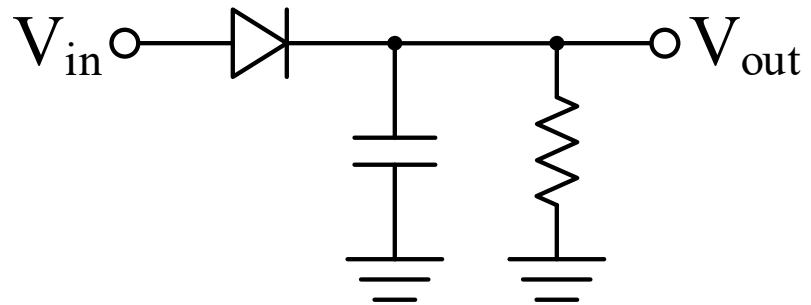


Signal Clamp (Limiter)

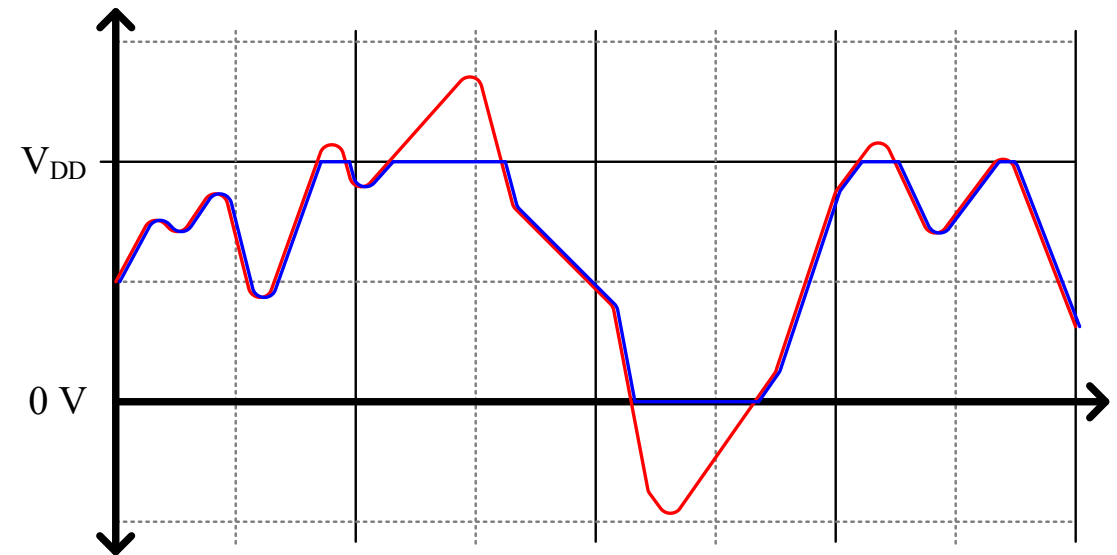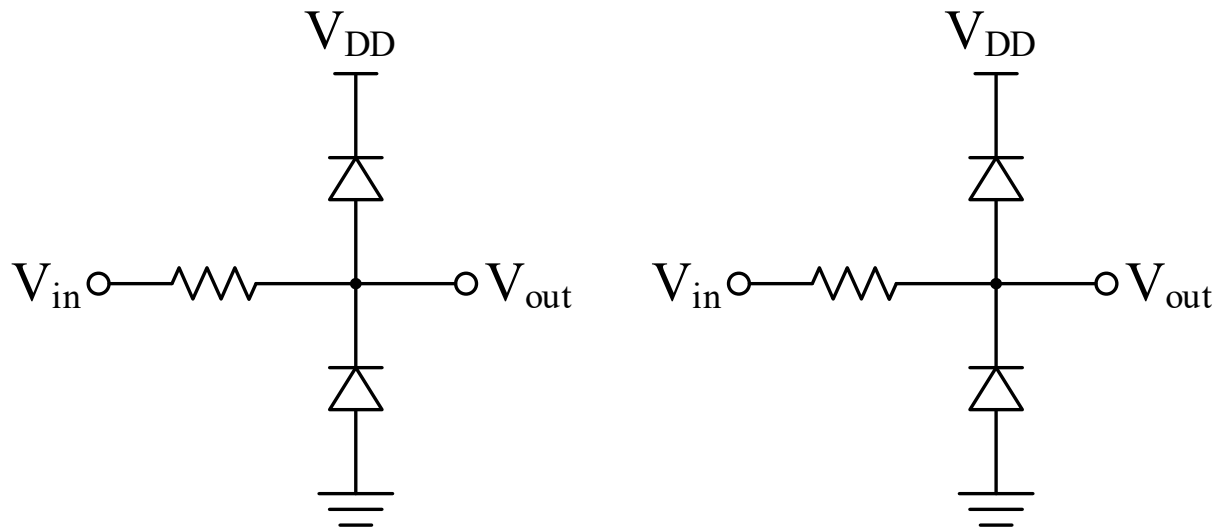- Signal voltages outside the rails can damage some components
- Diodes can limit such signals
 - Called “clamping” or “protection” diodes
 - Like a pressure release valve





“Ideal” Diode

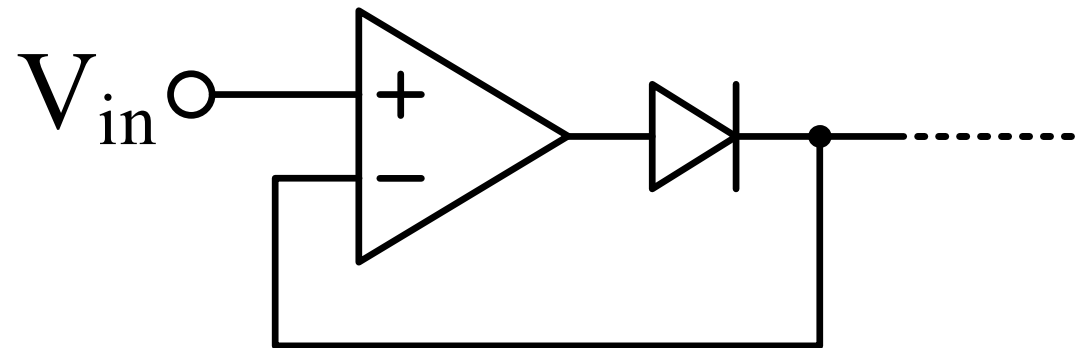- Feedback “cancels” opamp forward voltage drop



Protection for Inductive Kickback

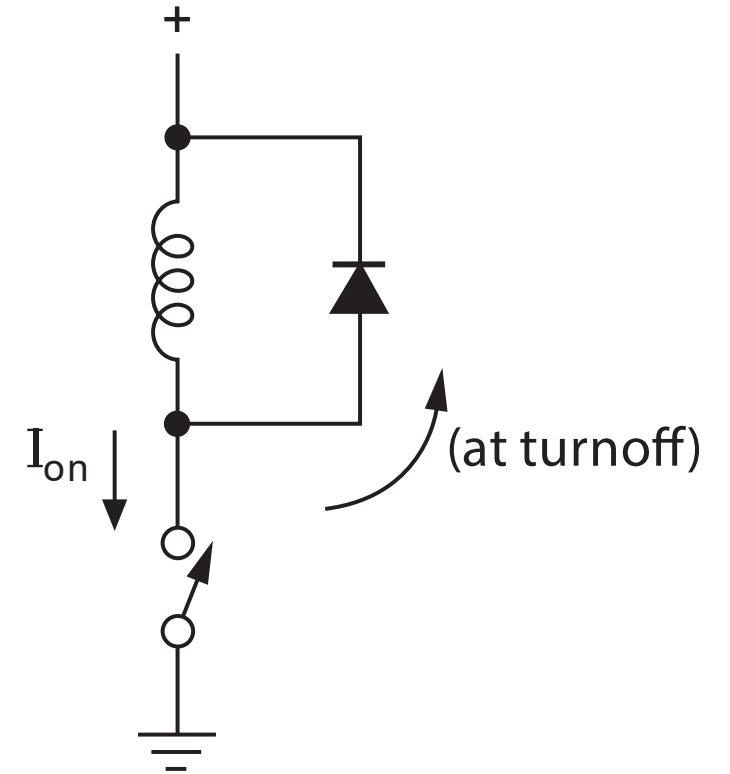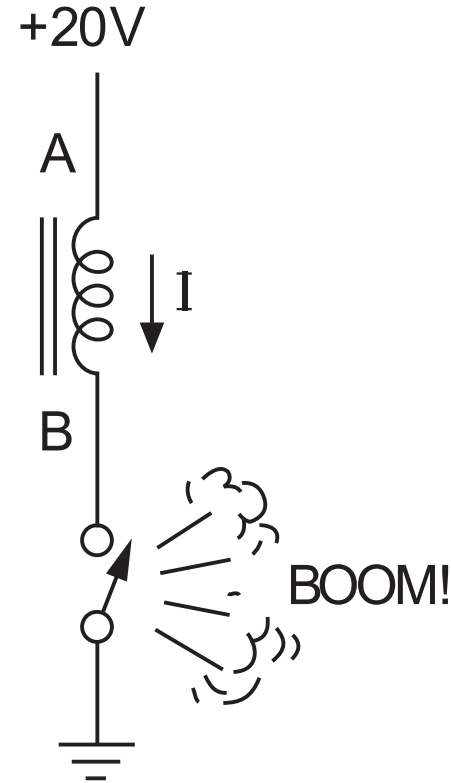- Recall how inductors react to dI/dt
- Diode gives safe pathway for magnetic field to discharge



LTSpice Modeling Challenge



- Create an opamp circuit that drives an LED current I_D based on an input voltage V_{set} and works regardless of variation in V_F
 - Using your new deeper understanding of opamps in closed-loop negative feedback to control I_D
 - Assume you have a precision resistor of your choosing
 - Choose an LED from Digikey
 - See if you can find an opamp model in LTSpice that is appropriate for your application (can it drive the required I_F ?)
 - Can you model V_{set} as a potentiometer wiper voltage (hint: “.param”)

