
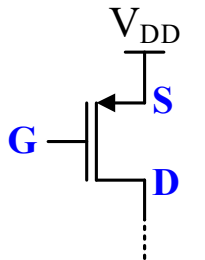
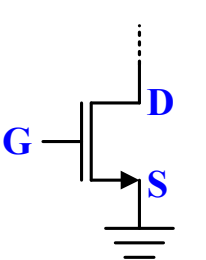
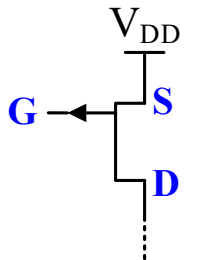
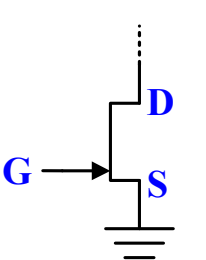
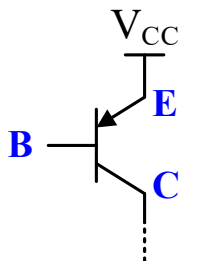
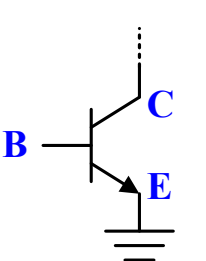




2.4.2 – Transistors Types

Types of Transistors

	P-Type	N-Type	Notes
MOSFET			
JFET			
BJT			

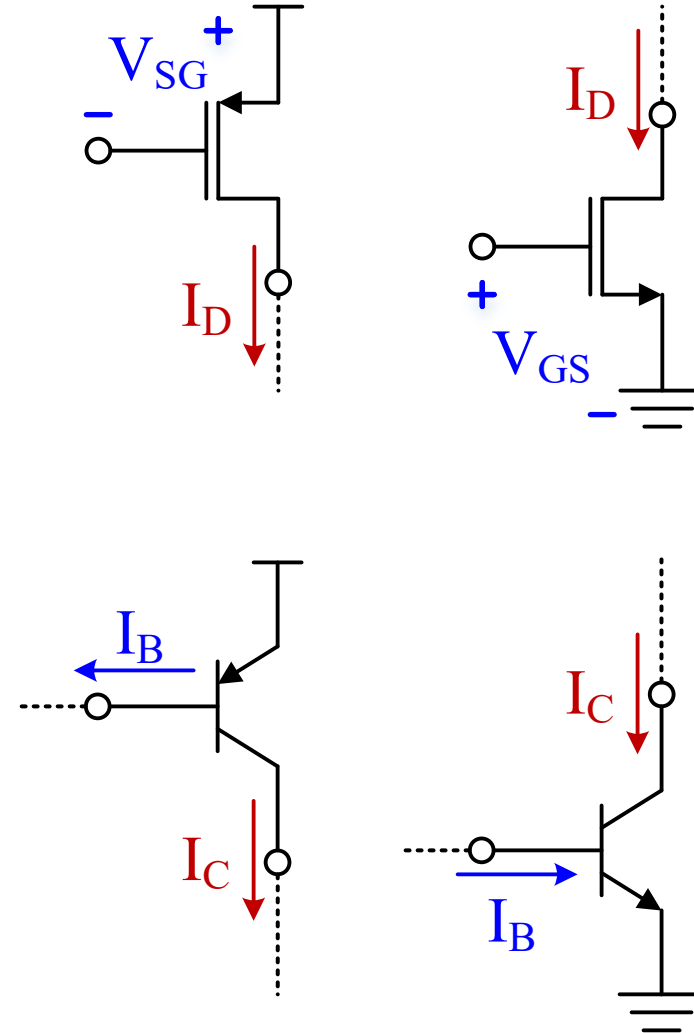

Using a BJT

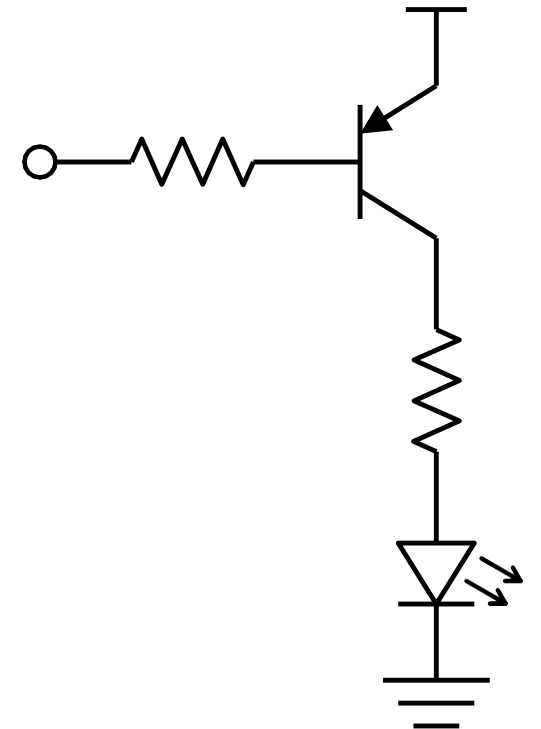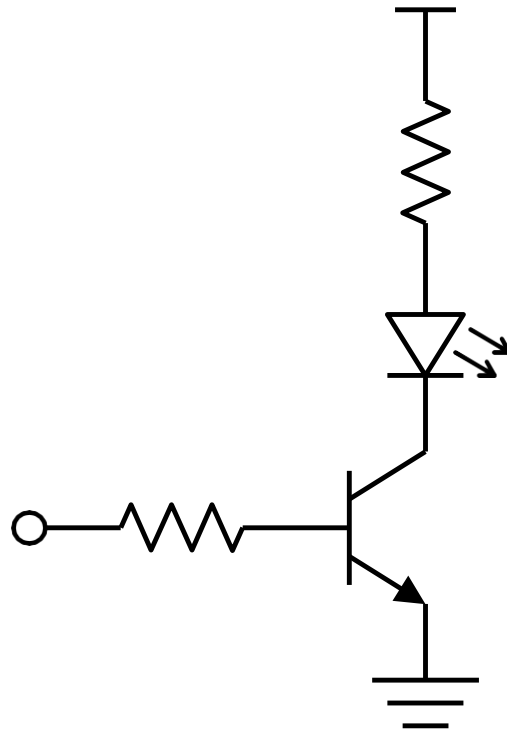

Example: Driving a Large Current

